

48521 FUNDAMENTALS of ELECTRICAL ENGINEERING

LECTURE 9A


The MOSFET (Metal-Oxide-Semiconductor Field-Effect Transistor)

5/5/2010

48521 Fundamentals of Elec
Eng: The MOSFET

1

MOSFET: physical structure

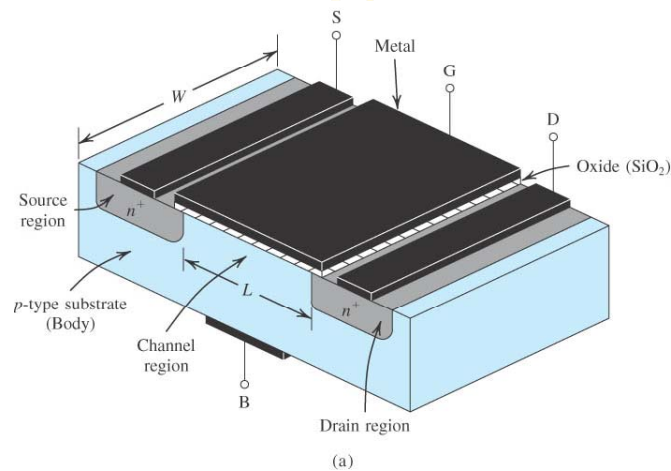


5/5/2010

48521 Fundamentals of Elec Eng:
The MOSFET

2

MOSFET (n-channel): operation

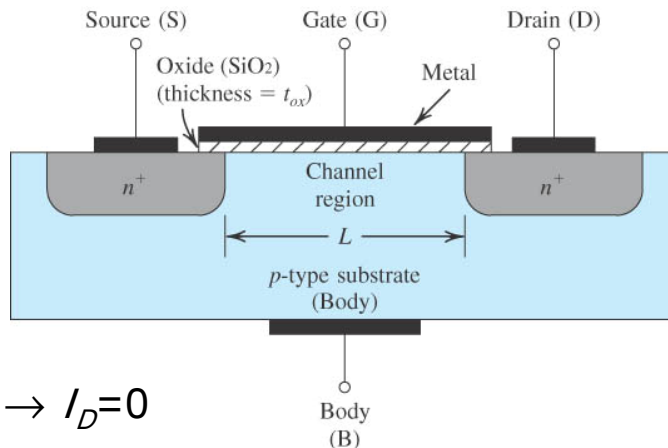

□ $V_{GS} \leq V_T \rightarrow I_D = 0$


5/5/2010

48521 Fundamentals of Elec Eng:
The MOSFET

3

MOSFET (n-channel): operation

□ $V_{GS} > V_T$

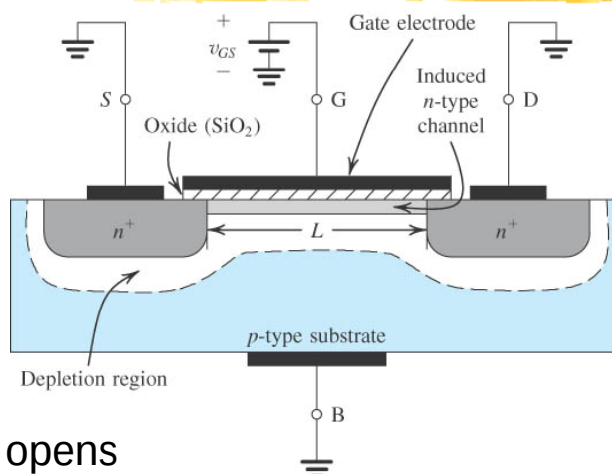

□ A channel opens


5/5/2010

48521 Fundamentals of Elec Eng:
The MOSFET

4

MOSFET (n-channel): operation

Small V_{DS} :

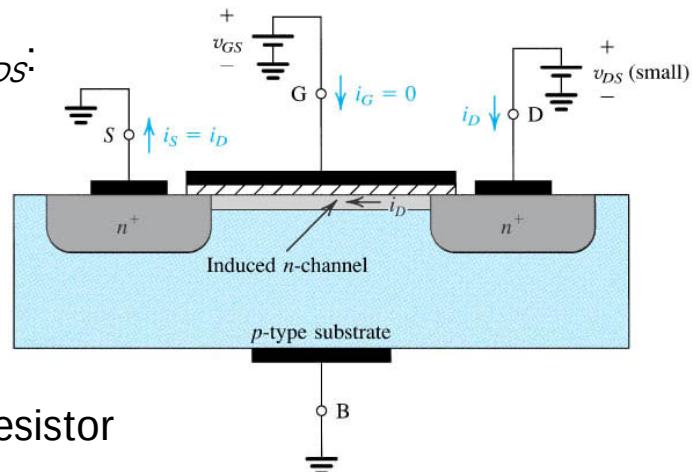

Linear resistor

5/5/2010

48521 Fundamentals of Elec Eng:
The MOSFET

5

MOSFET (n-channel): operation

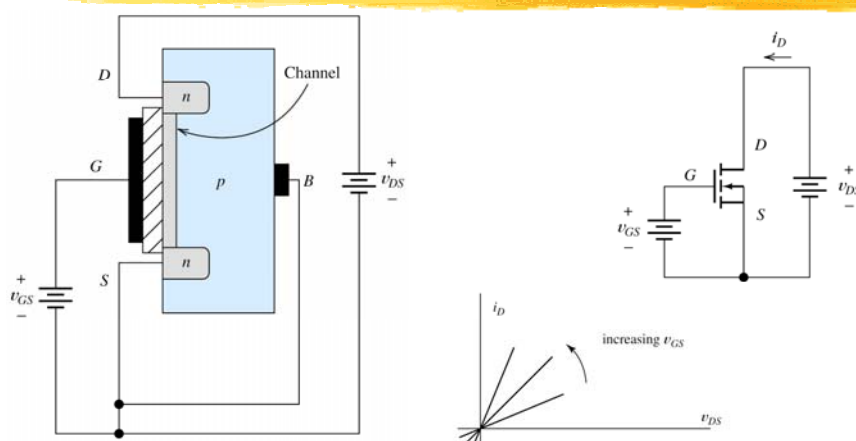


Figure 12.4 For $v_{GS} > V_{th}$, a channel of n -type material is induced in the region under the gate. As v_{GS} increases, the channel becomes thicker. For small values of v_{DS} , i_D is proportional to v_{DS} . The device behaves as a resistance whose value depends on v_{GS} .


5/5/2010

MOSFET (n-channel): operation

□ Larger V_{DS} :

□ Near the drain
channel shallows

□ $\rightarrow I_D$ saturates

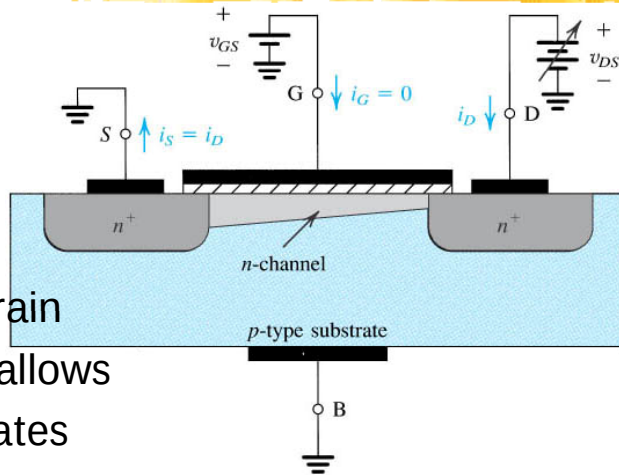

5/5/2010

48521 Fundamentals of Elec Eng:
The MOSFET

7

MOSFET: output characteristics

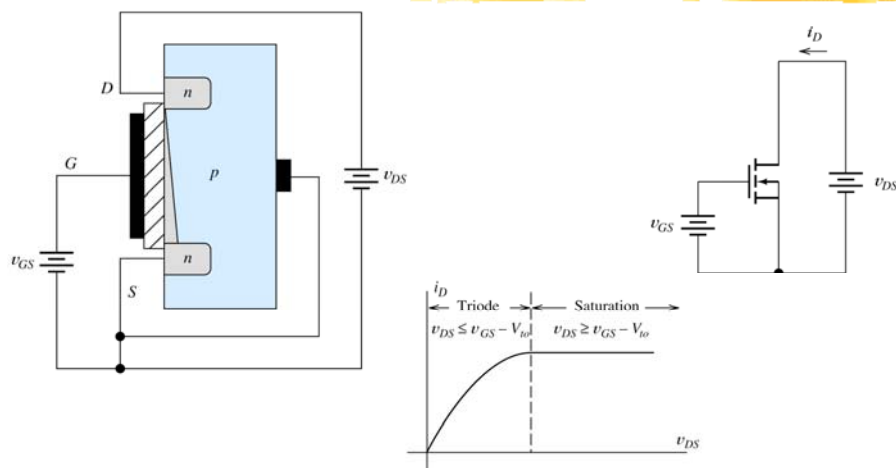


Figure 12.5 As v_{DS} increases, the channel pinches down at the drain end and i_D increases more slowly. Finally, for $v_{DS} > v_{GS} - V_{th}$, i_D becomes constant.

5/5/2010

8

MOSFET: output characteristics

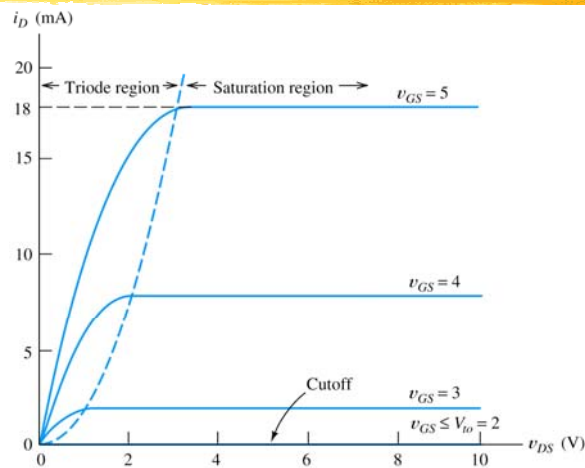



Figure 12.6 Characteristic curves for an NMOS transistor.

5/5/2010

The MOSFET

9

FET: transfer characteristics

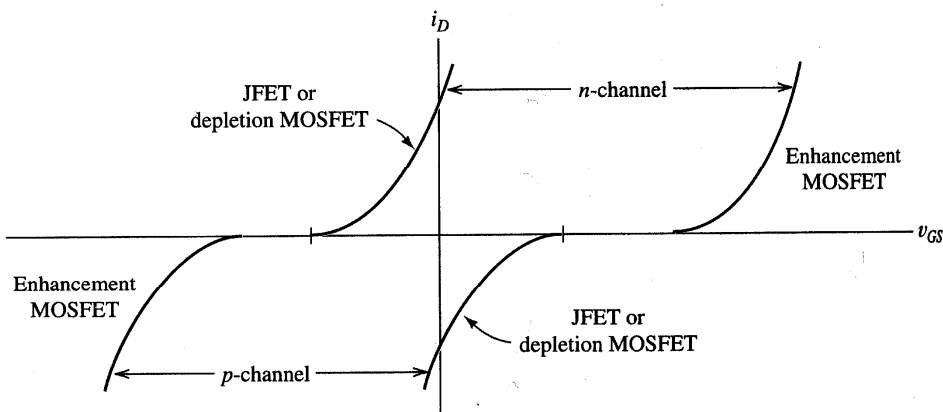


48521 Fundamentals of Elec Eng:
The MOSFET

5/5/2010

10

FET: circuit symbols

□ *p*-channel devices:

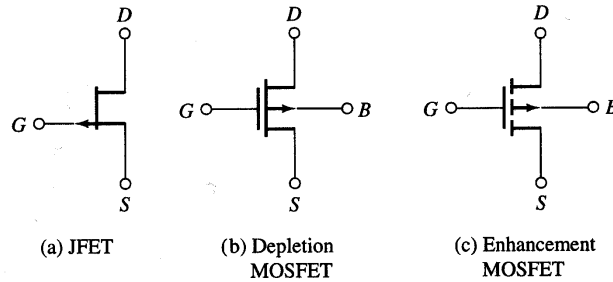

□ For *n*-channel devices, reverse the arrows

5/5/2010

48521 Fundamentals of Elec Eng:
The MOSFET

11

FET Model (Large-Signal)

□ Both FETs (JFET and MOSFET) can be described by mathematically identical equations:

$$i_D = \begin{cases} K[2(v_{GS} - V_t) - v_{DS}]v_{DS} ; v_{DS} \leq v_{GS} - V_t \\ K(v_{GS} - V_t)^2 ; v_{DS} > v_{GS} - V_t \end{cases}$$

5/5/2010

48521 Fundamentals of Elec Eng:
The MOSFET

12

FET Model (Large-Signal)

□ For JFETs: $K \leftarrow \frac{I_{DSS}}{V_p^2}$; $V_t \leftarrow V_p$ (pinch – off voltage)

□ For MOSFETs: $K \leftarrow \frac{\mu C_{ox}}{2} \frac{W}{L}$

μ – carrier mobility

C_{ox} – oxide capacitance [F/m^2]

W, L - channel width and length

MOSFET: biasing

- Voltage divider
- Drain-Gate feedback
- Current source
- Self-bias
- Zero-bias (depletion type only)

MOSFET biasing: voltage divider

- $R_G = R_1 R_2 / (R_1 + R_2)$
- R_G very large ($\sim \text{M}\Omega$)
- $i_G = 0 \rightarrow$
- $\rightarrow V_G = V_{DD} R_2 / (R_1 + R_2)$
- $i_G = 0 \rightarrow i_D = i_S$
- $V_{GS} = V_G - i_D R_S$
- $V_{DS} = V_{DD} - i_D (R_D + R_S)$

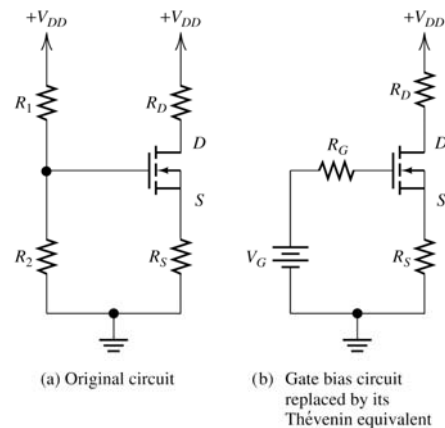


Figure 12.13 Fixed-bias plus self-bias circuit.

48521 Fundamentals of Elec Eng:
The MOSFET

5/5/2010

15

MOSFET biasing: voltage divider

- To find the operating point we usually assume that the device operates in the saturation region, i.e.:

$$i_D = K(v_{GS} - V_t)^2$$

- But we also have:

$$v_{GS} = V_G - i_D R_S ; \quad v_{GS} > V_t$$

48521 Fundamentals of Elec Eng:
The MOSFET

5/5/2010

16

MOSFET biasing: voltage divider

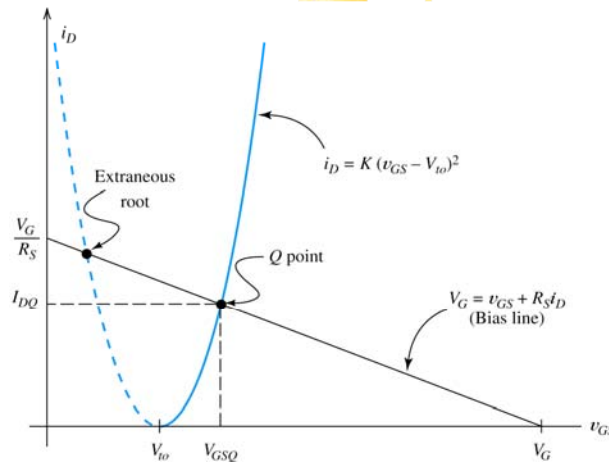


Figure 12.14 Graphical solution of Equations 12.12 and 12.13.

5/5/2010

The MOSFET

17

MOSFET biasing: voltage divider

□ Now, we have to solve for v_{GS} :

$$V_G = v_{GS} + R_S K (v_{GS} - V_t)^2$$

□ or

$$R_S K v_{GS}^2 + (1 - 2V_t R_S K) v_{GS} + R_S K V_t^2 - V_G = 0$$

□ This quadratic equation has two solutions;
we must accept only $v_{GS} > V_t$

5/5/2010

48521 Fundamentals of Elec Eng:
The MOSFET

18

MOSFET biasing: voltage divider

- Once v_{GS} is known, we calculate i_D :

$$i_D = K(v_{GS} - V_t)^2$$

- and $v_{DS} = V_{DD} - i_D(R_D + R_S)$

- Finally, we must check if $v_{DS} > v_{GS} - V_t$

- If not, the MOSFET is NOT in saturation !

- Repeat, assuming triode (linear) region.


5/5/2010

48521 Fundamentals of Elec Eng:
The MOSFET

19

MOSFET biasing: drain-gate feedback

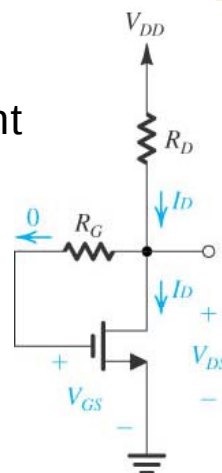- Here $v_{GS} = v_{DS}$
- In an n -channel enhancement MOSFET $V_t > 0$
- So, the saturation condition $v_{DS} > v_{GS} - V_t$ is **always** satisfied
- $v_{DS} = V_{DD} - R_D K (v_{DS} - V_t)^2$




5/5/2010

48521 Fundamentals of Elec Eng:
The MOSFET

20

MOSFET biasing: current source (mirror)

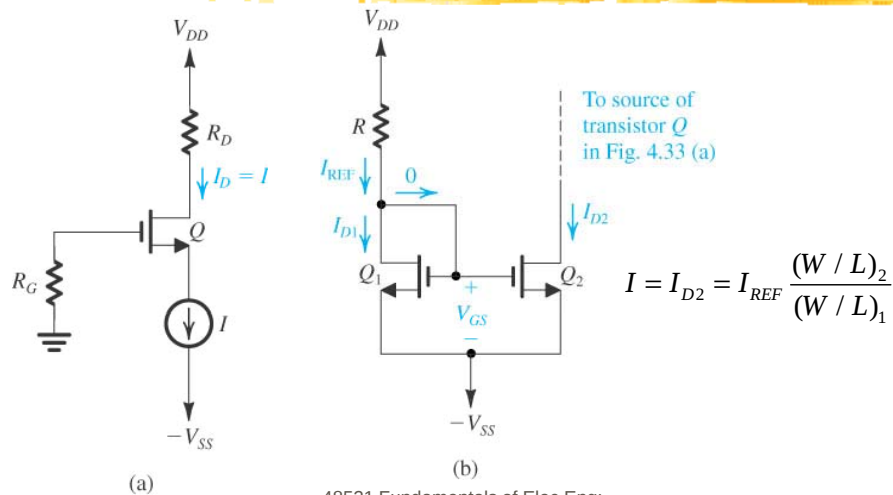

5/5/2010

48521 Fundamentals of Elec Eng:
The MOSFET

21