

48521 FUNDAMENTALS of ELECTRICAL ENGINEERING

LECTURE 10A

MOSFET Voltage Amplifiers

5/10/2010

48521 Fundamentals of Elec
Eng: MOSFET Amplifiers

1

MOSFET : Small-Signal Model

□ Like for other semiconductor devices, to obtain a small-signal model, we linearise around the operating (quiescent) point:

$$g_m = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_{v_{DS}=V_{DSQ}} = \begin{cases} 2\sqrt{KI_{DQ}} ; & \text{in saturation} \\ 2KV_{DSQ} ; & \text{in triode region} \end{cases}$$

5/10/2010

48521 Fundamentals of Elec Eng:
MOSFET Amplifiers

2

MOSFET : Small-Signal Model

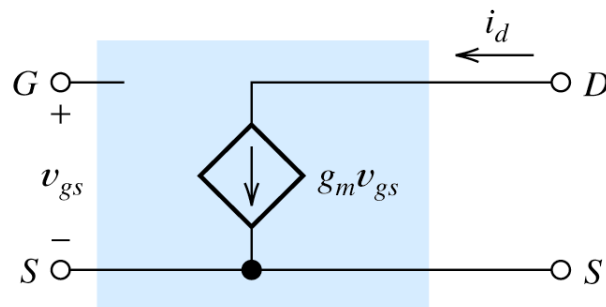


Figure 12.19 Small-signal equivalent circuit for FETs.


5/10/2010

48521 Fundamentals of Elec Eng:
MOSFET Amplifiers

3

MOSFET : Small-Signal Model

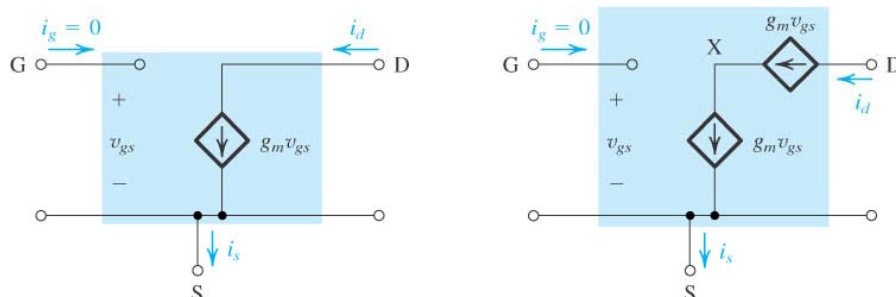Development of the T equivalent circuit model




5/10/2010

48521 Fundamentals of Elec Eng:
MOSFET Amplifiers

4

MOSFET : Small-Signal Model

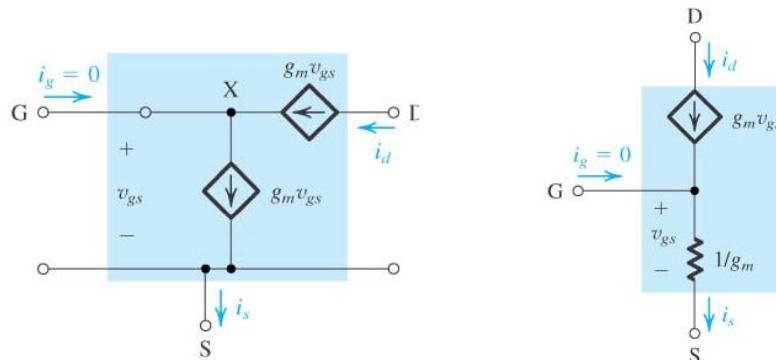Development of the T equivalent circuit model




5/10/2010

48521 Fundamentals of Elec Eng:
MOSFET Amplifiers

5

MOSFET : real characteristic

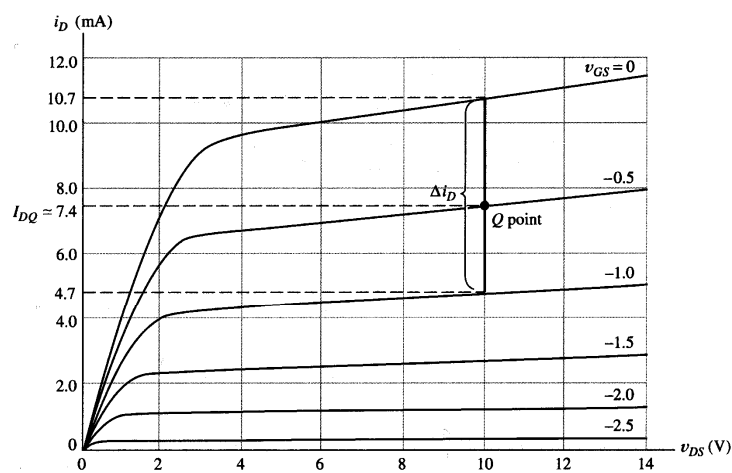

5/10/2010

48521 Fundamentals of Elec Eng:
MOSFET Amplifiers

6

MOSFET : Improved s-s Model

- To account for a nonzero slope in saturation, we add the output resistance r_d (or r_o)

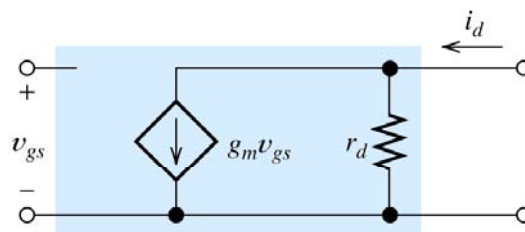


Figure 12.20 FET small-signal equivalent circuit that accounts for the dependence of i_D on v_{DS} .


5/10/2010

48521 Fundamentals of Elec Eng:
MOSFET Amplifiers

7

MOSFET : Improved s-s Model

T version

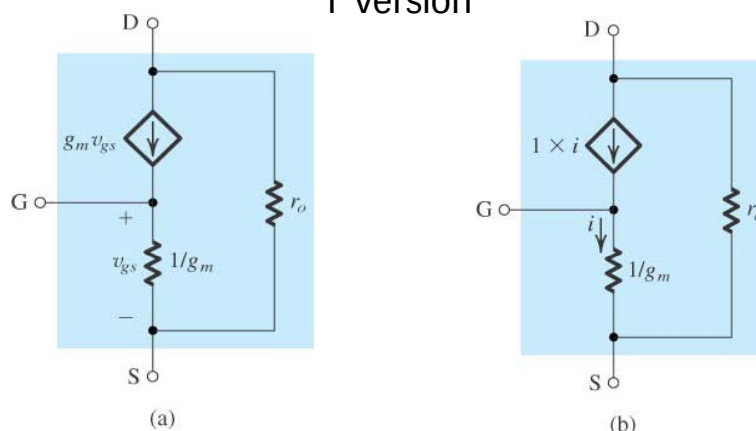

5/10/2010

48521 Fundamentals of Elec Eng:
MOSFET Amplifiers

8

Common-Source Amplifier

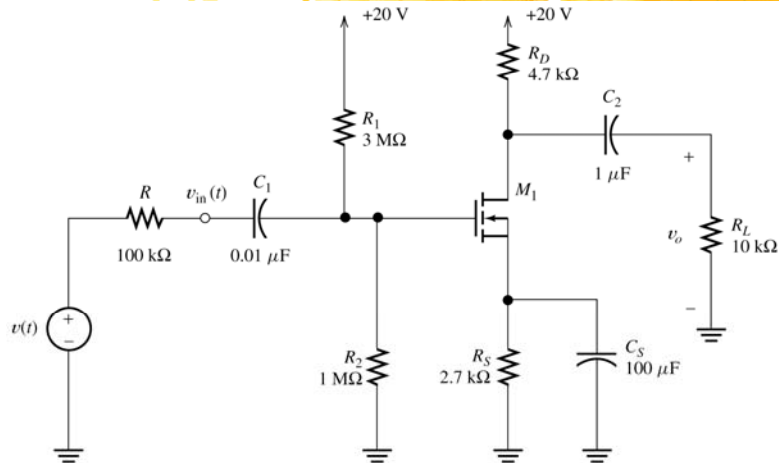



Figure 12.25 Common-source amplifier.
MOSFET Amplifiers

5/10/2010

9

Common-Source Amplifier

Typical frequency response:

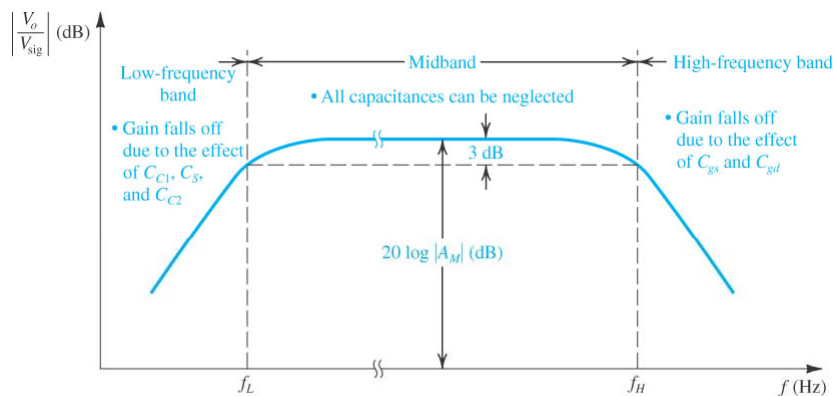

5/10/2010

48521 Fundamentals of Elec Eng:
MOSFET Amplifiers

10

Common-Source Amplifier

- ❑ To obtain a *midband* small-signal equivalent circuit:
 - short-circuit all by-pass and coupling cap's
 - short-circuit all independent voltage sources
 - open-circuit all independent current sources
 - replace transistors by their small-signal models
 - re-draw the circuit


5/10/2010

48521 Fundamentals of Elec Eng:
MOSFET Amplifiers

11

Common-Source Amplifier

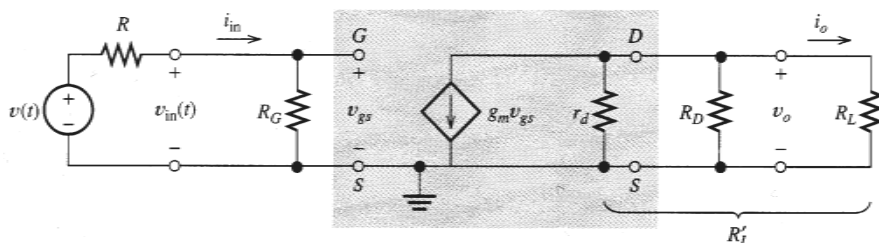- ❑ Midband Small-Signal Equivalent Circuit:



- ❑ Note that $v_{gs} = v_{in}$

5/10/2010

48521 Fundamentals of Elec Eng:
MOSFET Amplifiers

12

Common-Source Amplifier

□ Voltage transmittance (voltage gain):

$$A_v = \frac{v_o}{v_{in}}; \quad v_{gs} = v_{in}$$

$$v_o = -g_m v_{gs} R'_L = -g_m v_{in} (r_d \parallel R_D \parallel R_L)$$

$$A_v = -g_m (r_d \parallel R_D \parallel R_L)$$


5/10/2010

48521 Fundamentals of Elec Eng:
MOSFET Amplifiers

13

Common-Source Amplifier

□ Output Resistance:

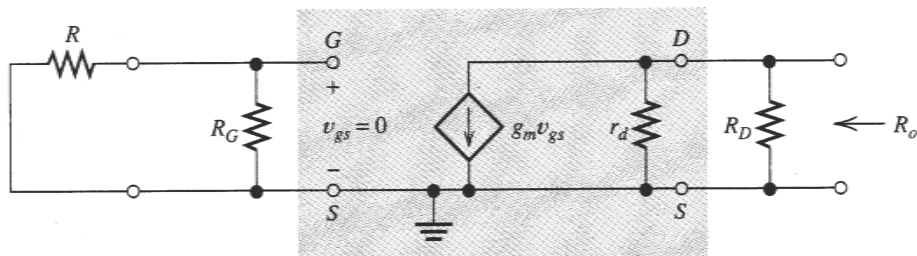

$$\square v_{gs} = 0 \rightarrow g_m v_{gs} = 0 \rightarrow R_o = r_d \parallel R_D$$

5/10/2010

48521 Fundamentals of Elec Eng:
MOSFET Amplifiers

14

Common-Drain Amplifier (Source Follower)

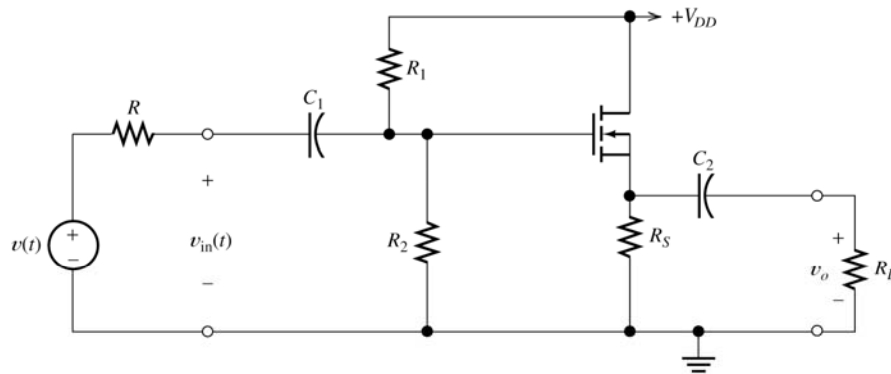


Figure 12.26 Source follower.

48521 Fundamentals of Elec Eng:
MOSFET Amplifiers

5/10/2010

15

Source Follower: voltage gain

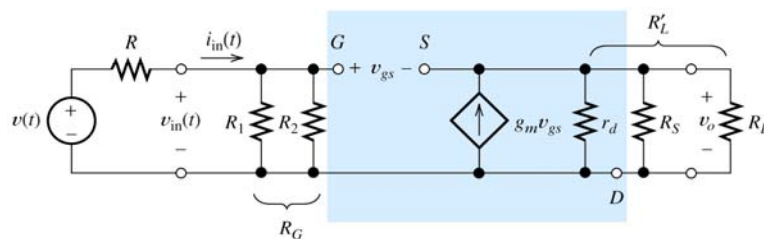


Figure 12.27 Small-signal ac equivalent circuit for the source follower.

$$v_o = g_m v_{gs} (r_d \parallel R_S \parallel R_L) = g_m v_{gs} R'_L$$

$$v_{gs} = v_{in} - v_o$$

$$v_o = g_m (v_{in} - v_o) R'_L$$

$$A_v = \frac{v_o}{v_i} = \frac{g_m R'_L}{1 + g_m R'_L}$$

48521 Fundamentals of Elec Eng:
MOSFET Amplifiers

5/10/2010

16

Source Follower: R_{out}

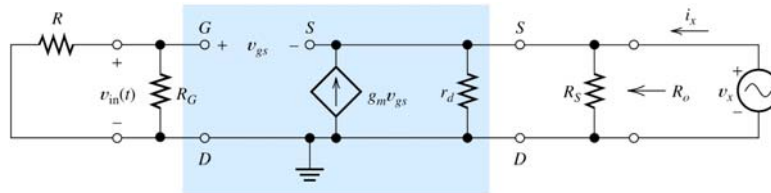


Figure 12.28 Equivalent circuit used to find the output resistance of the source follower.

$$v_{gs} = v_g - v_s = 0 - v_x = -v_x$$

$$i_x = \frac{v_x}{R_S} + \frac{v_x}{r_d} + v_x g_m$$

$$R_o = \frac{v_x}{i_x} = \frac{1}{\frac{1}{R_S} + \frac{1}{r_d} + g_m}$$

5/10/2010

48521 Fundamentals of Elec Eng:
MOSFET Amplifiers

17