

48521 FUNDAMENTALS of ELECTRICAL ENGINEERING

LECTURE 11A

The BJT (Bipolar Junction Transistor)

5/17/2010

48521 Fundamentals of Elec
Eng: The BJT

1

N-P-N Bipolar Junction Transistor

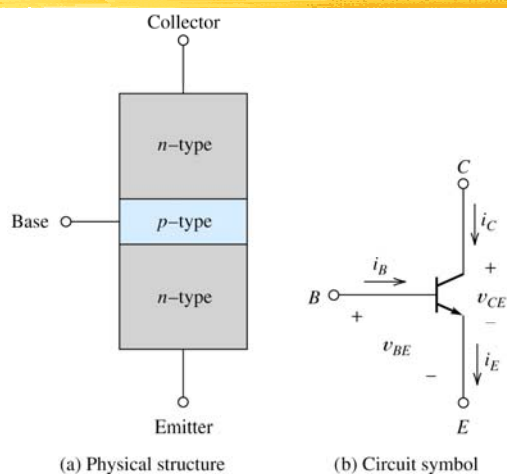


Figure 13.1 The *n*pn BJT.
The BJT

5/17/2010

2

N-P-N Bipolar Junction Transistor

- In **normal** operation, B-E junction is biased in forward and B-C junction is biased in reverse.
- Emitter current i_E is given by Shockley's equation:

$$i_E = I_{ES} \left[\exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right]$$

5/17/2010

48521 Fundamentals of Elec Eng:
The BJT

3

N-P-N Bipolar Junction Transistor

- The KCL requires that $i_E = i_C + i_B$
- Introducing the parameter $\alpha = i_C/i_E$ we can write:

$$i_C = \alpha I_{ES} \left[\exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right]$$

and:

$$i_B = (1 - \alpha)i_E \quad i_B = (1 - \alpha)I_{ES} \left[\exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right]$$

5/17/2010

48521 Fundamentals of Elec Eng:
The BJT

4

N-P-N Bipolar Junction Transistor

□ Defining the parameter $\beta = i_C/i_B = \alpha/(1 - \alpha)$, we have: $i_C = \beta i_B$

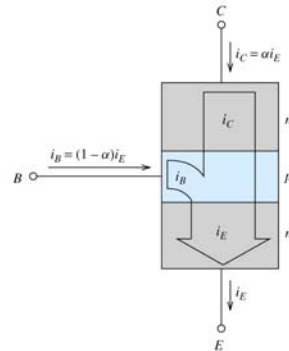


Figure 13.3 Only a small fraction of the emitter current flows into the base (provided that the collector-base junction is reverse biased and the base-emitter junction is forward biased).

5/17/2010

48521

The BJT

5

Common-Emitter Characteristics

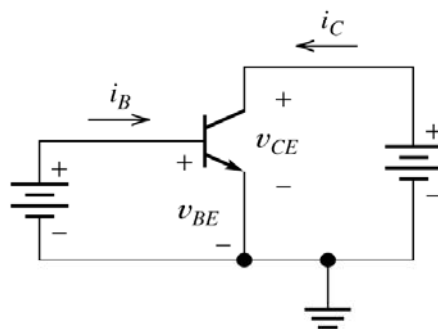


Figure 13.4 Common-emitter circuit configuration for the npn BJT.

5/17/2010

48521 Fundamentals of Elec Eng:
The BJT

6

Common-Emitter Characteristics

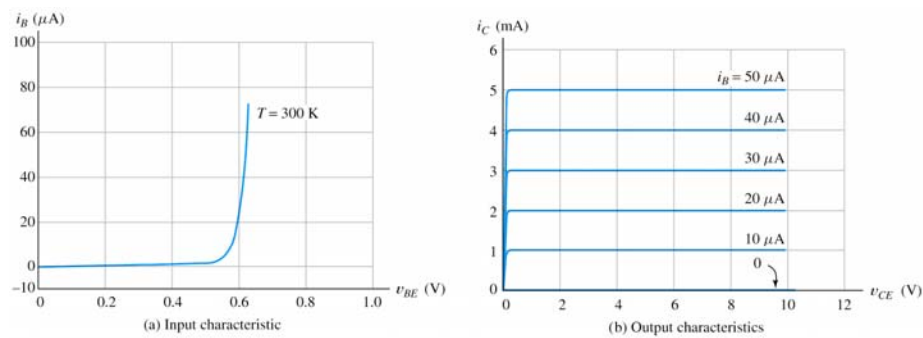



Figure 13.5 Common-emitter characteristics of a typical *nnp* BJT.

5/17/2010

48521 Fundamentals of Elec Eng:
The BJT


7

P-N-P Device

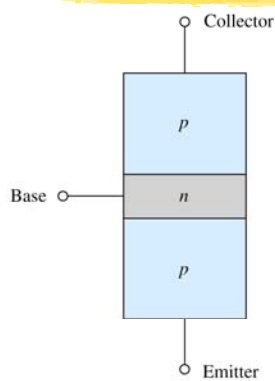

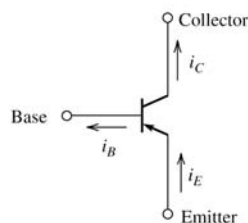(a) Physical structure

All equations are the same as for p-n-p device if we reverse the polarity of v_{BE} and v_{BC}



(b) Circuit symbol with reference directions for currents

Figure 13.13 The *pnp* BJT.

5/17/2010

48521 Fundamentals of Elec Eng:
The BJT

8

BJT: Regions of Operation

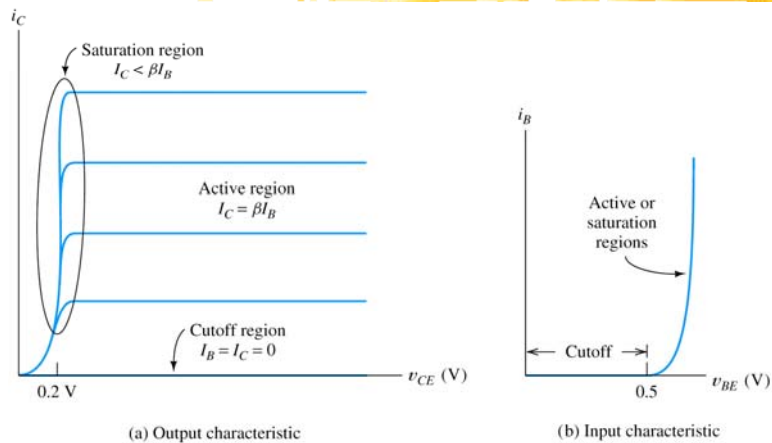


Figure 13.17 Regions of operation on the characteristics of an *nnp* BJT.


48521 Fundamentals of Elec Eng:
The BJT

5/17/2010

9

Large-Signal Models

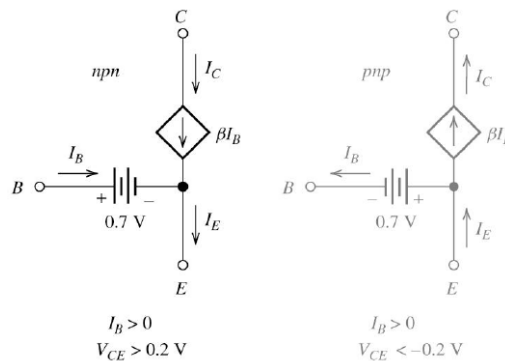□ Normal Active Region: **B-E - fwd, B-C - rev.**




5/17/2010

48521 Fundamentals of Elec Eng:
The BJT

10

Large-Signal Models

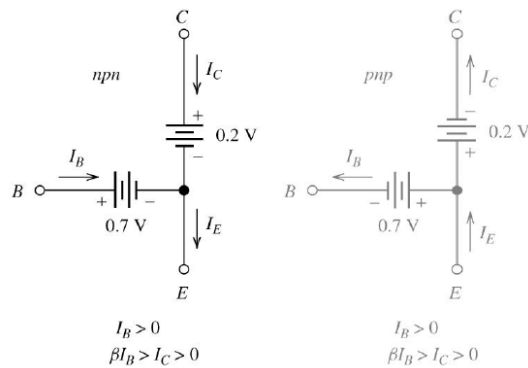□ Saturation Region: **B-E - fwd, B-C - fwd**




5/17/2010

48521 Fundamentals of Elec Eng:
The BJT

11

Large-Signal Models

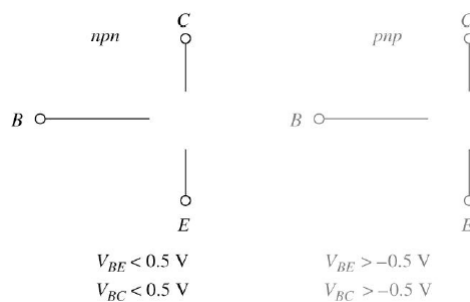□ Cut-off Region: **B-E - rev., B-C - rev.**



5/17/2010

48521 Fundamentals of Elec Eng:
The BJT

12

DC Analysis of BJT Circuits

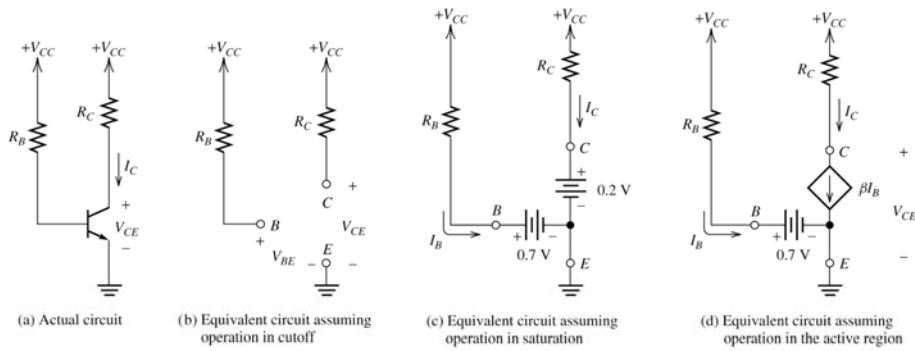



Figure 13.18 Bias circuit of Examples 13.4 and 13.5.

5/17/2010

48521 Fundamentals of Elec Eng:
The BJT

13

DC Analysis of BJT Circuits

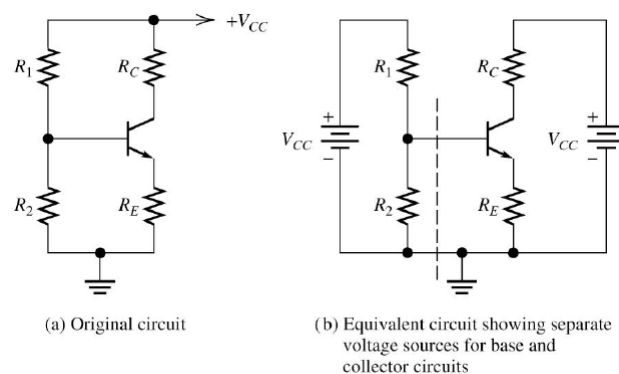


5/17/2010


48521 Fundamentals of Elec Eng:
The BJT

14

DC Analysis of BJT Circuits

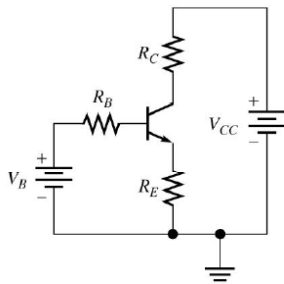

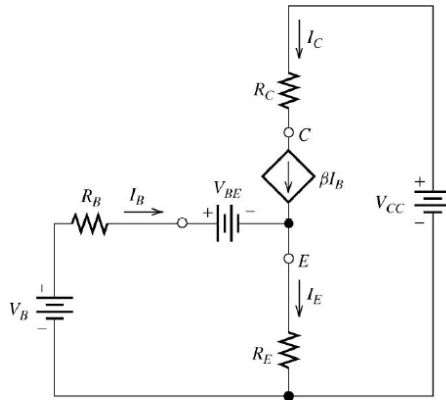(c) Circuit using Thévenin equivalent in place of V_{CC} , R_1 , and R_2




(d) Equivalent to part (c) with active-region transistor model

5/17/2010

48521 Fundamentals of Elec Eng:
The BJT

15

DC Analysis of BJT Circuits

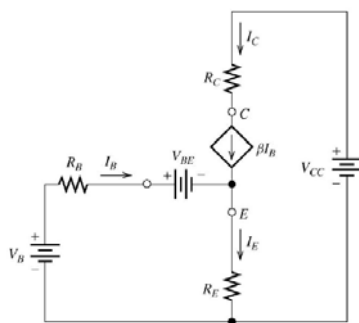

(d) Equivalent to part (c) with active-region transistor model

KVL in a B-E loop gives:

$$V_B = I_B R_B + V_{BE} + I_E R_E$$

But $I_E = (\beta + 1)I_B$, so:

$$V_B = I_B R_B + V_{BE} + (\beta + 1)I_B R_E$$

$$V_{BE} + [R_B + (\beta + 1)R_E]I_B$$


$$V_{CE} = V_{CC} - R_C I_C - R_E I_E$$

$$I_B = \frac{V_B - V_{BE}}{R_B + (\beta + 1)R_E}$$

5/17/2010

48521 Fundamentals of Elec Eng:
The BJT

16

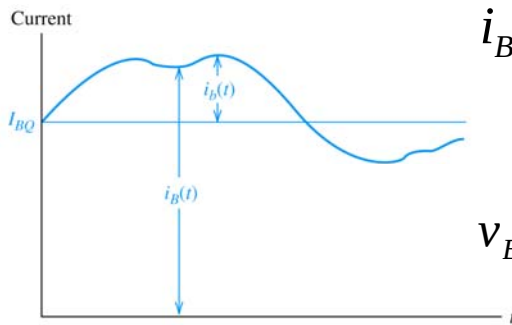

$$i_B(t) = I_{BQ} + i_b(t)$$

$$v_{BE}(t) = V_{BEQ} + v_{be}(t)$$

$i_b(t)$ denotes the signal current flowing into the base, I_{BQ} is the dc current that flows when the signal is absent, and $i_B(t)$ is the total base current. Similar notation is used for the other currents and voltages.


5/17/2010

48521 Fundamentals of Elec Eng:
The BJT

17

BJT: Small-Signal Model (hybrid- π)

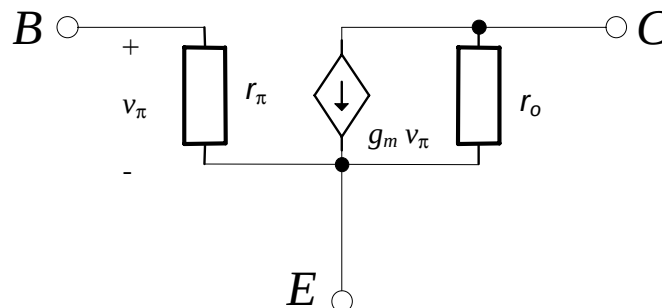There are three mathematically identical models with different topology. Model 1 (with transconductance g_m):




5/17/2010

48521 Fundamentals of Elec Eng:
The BJT

18

BJT: Small-Signal Model

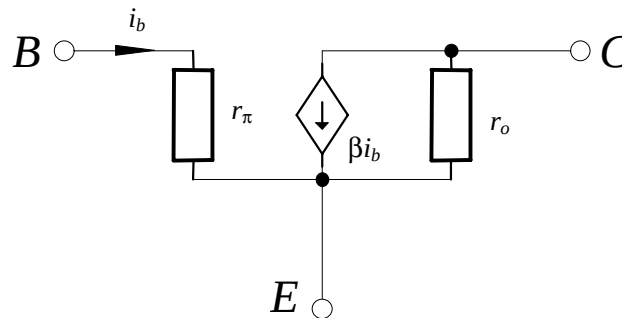There are three mathematically identical models with different topology. Model 2 (with CCCS βi_b):




5/17/2010

48521 Fundamentals of Elec Eng:
The BJT

19

BJT: Small-Signal Model

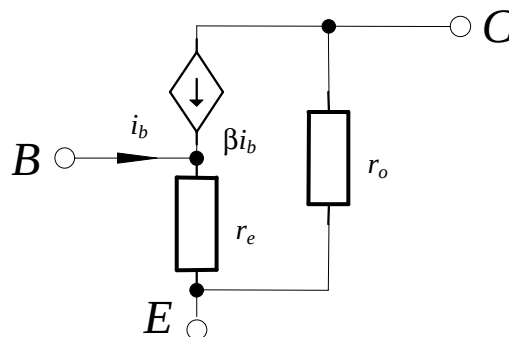There are three mathematically identical models with different topology. Model 3 (with emitter resistance r_e):



5/17/2010

48521 Fundamentals of Elec Eng:
The BJT

20

BJT: Small-Signal Model (hybrid- π)

The values of the basic elements of these models depend on the BJT parameters and the operating point.

$$g_m = \frac{I_{CQ}}{V_T} \quad r_\pi = \frac{\beta}{g_m} \quad r_e = \frac{\alpha}{g_m} \quad r_o = \frac{V_A}{I_{CQ}}$$

Where: I_{CQ} – quiescent collector current

V_T – thermal voltage (~ 26 mV)

V_A – Early voltage (~ 100 V)

β – transistor's current gain


$\alpha = \beta / (\beta + 1)$

5/17/2010

48521 Fundamentals of Elec Eng:
The BJT

21

Basic BJT Amplifiers Common Emitter

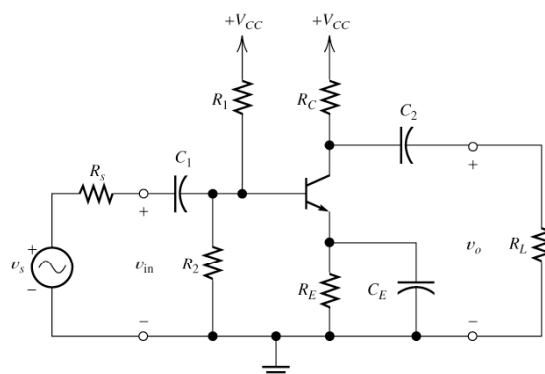

$$R_B = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$


5/17/2010

48521 Fundamentals of Elec Eng:
The BJT

22

Basic BJT Amplifiers Common Emitter

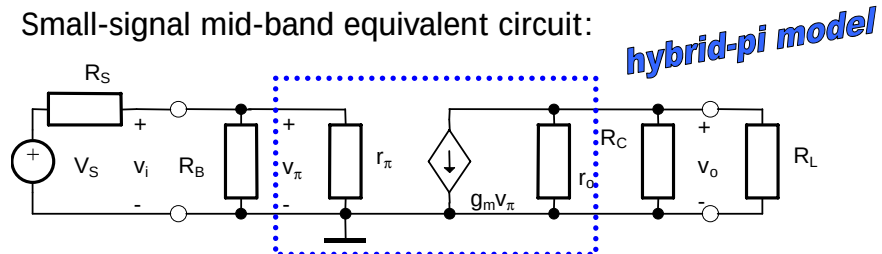Small-signal mid-band equivalent circuit:



Network functions:


$$A_v = \frac{v_o}{v_i} = \frac{-g_m}{G_C + g_o + G_L} \quad Z_{in} = \frac{1}{G_B + g_\pi} \quad Z_{out} = \frac{1}{G_C + g_o}$$

5/17/2010

48521 Fundamentals of Elec Eng:
The BJT

23

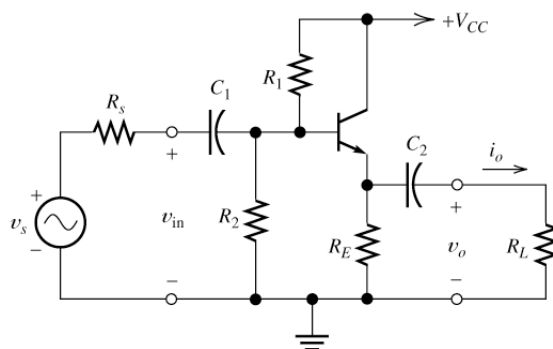Basic BJT Amplifiers Common Collector (Emitter Follower)



$$R_B = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

5/17/2010


48521 Fundamentals of Elec Eng:
The BJT

24

Basic BJT Amplifiers Common Collector (Emitter Follower)

Small-signal mid-band equivalent circuit:

hybrid-pi model

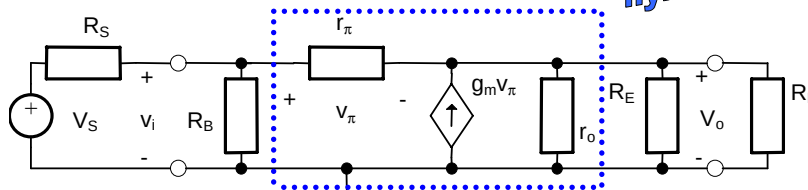

Network functions:

$$A_V = \frac{v_o}{v_i} = \frac{g_m + g_\pi}{g_m + g_\pi + G_E + g_o + G_L} \approx 1$$

$$Z_{in} = \frac{1}{G_B + g_\pi(1 - A_V)} \approx \frac{1}{G_B}$$


$$Z_{out} = \frac{1}{G_E + g_o + (g_m + g_\pi) \left(1 - \frac{g_\pi}{g_\pi + G_S + G_B} \right)}$$

5/17/2010

48521 Fundamentals of Elec Eng:
The BJT

25

Basic BJT Amplifiers Common Base

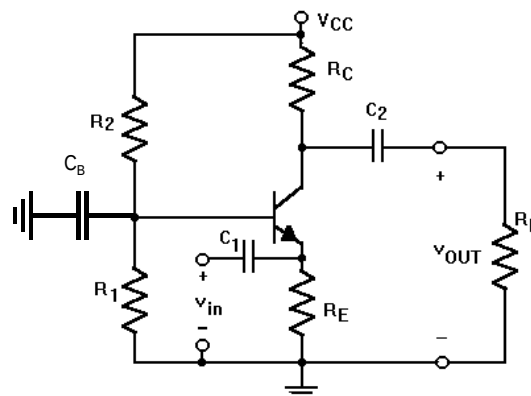

Common Base Amplifier

5/17/2010


48521 Fundamentals of Elec Eng:
The BJT

26

Basic BJT Amplifiers Common Base

Small-signal mid-band equivalent circuit:

hybrid-pi model

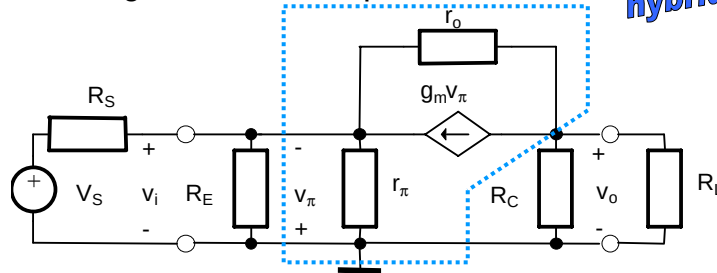

$$A_v = \frac{v_o}{v_i} = \frac{g_m + g_o}{G_C + g_o + G_L}$$

$$Z_{in} = \frac{1}{G_E + g_\pi + g_o(1 - A_v) - g_m}$$

5/17/2010

48521 Fundamentals of Elec Eng:
The BJT

27