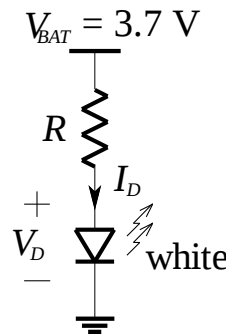


6 LED Driver Design


- (a) A simple circuit used to “drive” an LED is shown below. The three voltages correspond to minimum, typical and maximum “forward voltages” for the LED.

	V_D (V) (aka V_F)	I_D (mA) (aka I_F)	Relative luminous intensity (%)
	$V_{Dmin} =$		
	$V_{Dtyp} = 2.8$	20	100
	$V_{Dmax} =$		

- (i) Design the resistor R for the typical V_D and a current of $I_D = 20$ mA .
- (ii) Using information in the [LED datasheet](#), and using a constant voltage drop model for the LED, determine the min. and max. LED currents.
- (iii) Using Fig. 2 in the datasheet, estimate the relative luminous intensity.

What is the problem with this type of circuit for driving an LED?

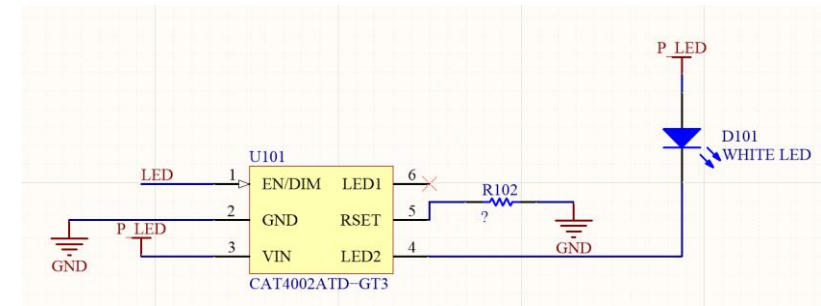- (b) Using information given in the [LED driver datasheet](#), design the following LED driver circuit so that the LED current is a constant 20 mA.



(This schematic is available as a separate PDF.)

There is a section on page 7 of the datasheet called “LED Current Selection”. Use this formula to determine R102.

Use a 1% (E96) resistor.

What is the advantage of this circuit for driving an LED?