

## Tutorial Answers

### 2B.1

2 C

### 2B.2

48 mΩ

### 2B.3

3.7 Ω

### 2B.5

10 V, -5 V

### 2B.6

$$i_C = -6 \text{ A}, i_E = -4 \text{ A}, i_F = 4 \text{ A}, i_G = 2 \text{ A}$$

# A.2

## 3B.1

(a)  $v_3 = 25 \text{ V}$

(b)  $I_s = 5/4 \text{ A}$

(c)  $I_3 = 5/12 \text{ A}$

## 3B.2

$v_1 = 20/3 \text{ V}$ ,  $v_2 = -10/3 \text{ V}$ ,  $I_s = 10/3 \text{ A}$

## 3B.3

$I_{20} = 2 \text{ A} \rightarrow$ ,  $I_{10} = 3 \text{ A} \downarrow$ ,  $I_{12} = 1 \text{ A} \leftarrow$ ,  $I_{14} = 2 \text{ A} \rightarrow$

**4A**

- (a) 2.52 V
- (b) 50.0 mA
- (c) 87.6 mW
- (d) 2.0 V
- (e) 43.8 mA

# A.4

## 4B.1

$$I_S = 10/3 \text{ A}$$

## 4B.2

(a)  $V_{Th} = 12 \text{ V}$ ,  $I_N = 12/5 \text{ A}$ ,  $R_{Th} = R_N = 5 \Omega$

(b)  $R_L = 5 \Omega$

(c)  $7.2 \text{ W}$



## 4B.3

(a)  $R_{Th} = 2 \text{ k}\Omega$

(b)  $V_{Th} = -6 \text{ V}$

(c)  $I_N = -3 \text{ mA}$

(d)

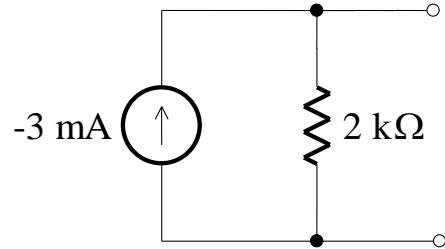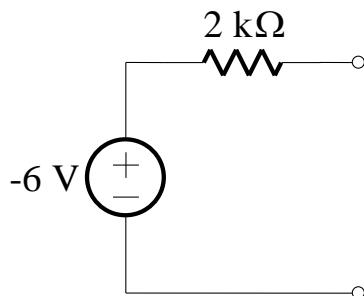

(e)  $I_L = -1 \text{ mA}$

(f)  $R_L = 2 \text{ k}\Omega$

(g)  $P_{L\max} = 9/2 \text{ mW}$



**5A**

- (h)  $R_{21} = 4\text{M}02, R_{22} = 16\text{M}0$
- (i)  $R_{23} = 5\text{M}49, R_{24} = 4\text{M}53$
- (j)  $R_{25} = 5\text{M}49, R_{26} = 4\text{M}53$
- (k)  $R_{27} = 680\text{k}, R_{28} = 6\text{M}2, R_{29} = 3\text{M}3$

# A.6

## 5B.1


(a)

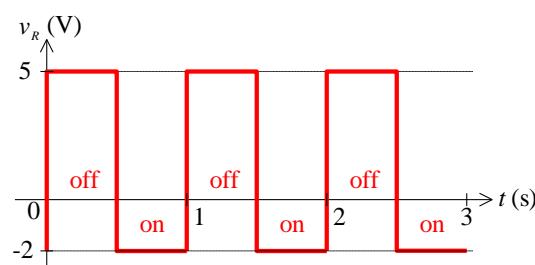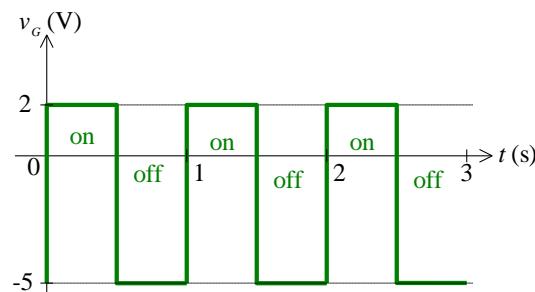


(b) The green and red LEDs would light alternately every second.

## 5B.2

(a)

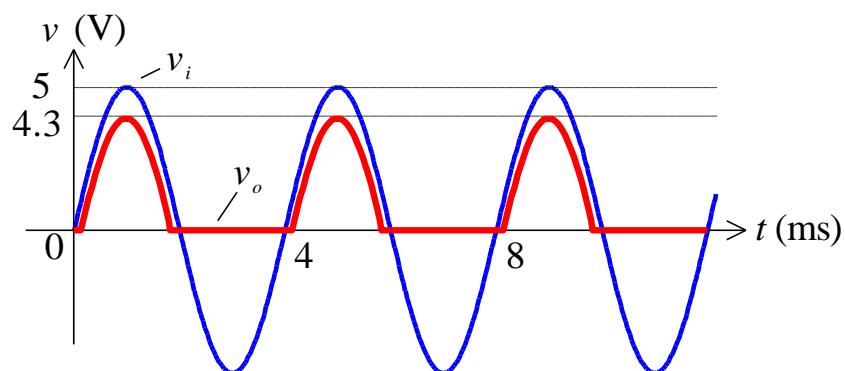

(b)  $\hat{I} = 4.3 \text{ mA}$

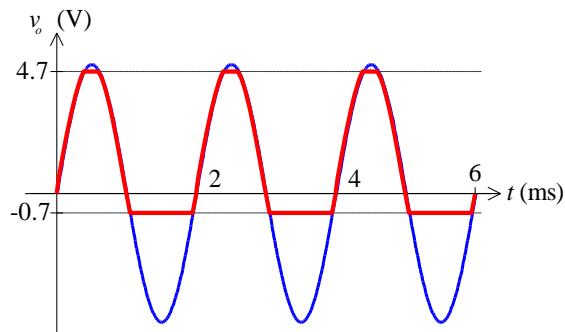**5B.3****5B.4**

Input protection from overvoltage, undervoltage and electrostatic discharge (ESD) events.

# A.8

## 6A

- (a) (i)  $R = 45 \Omega$       (ii)  $I_{D_{\min}} = 29 \text{ mA}$ ,  $I_{D_{\max}} = 11 \text{ mA}$       (iii) 60%

There is a large variation in output luminosity due to the variance of the LED characteristic.

- (b)  $R_{102} = 3k74$

This circuit sets a constant current, and therefore a constant luminosity of the LED.

**6B.1**

(a)  $2.46 \times 10^{-7} \angle -18.1^\circ \text{ N}$

(b)  $-18.1^\circ$

(c)  $24.6 \angle -18.1^\circ \text{ Vm}^{-1}$

**6B.2**

(a)  $\mathbf{E} = \frac{q}{4\pi\epsilon_0 r^2} \hat{\mathbf{r}}$ ,  $\hat{\mathbf{r}}$  points along a spherical radius

(b)  $\mathbf{E} = \mathbf{0}$

(c)  $\mathbf{E} = \frac{\lambda}{2\pi\epsilon_0 r} \hat{\mathbf{r}}$ ,  $\hat{\mathbf{r}}$  points along a cylindrical radius

(d)  $\mathbf{E} = \frac{\sigma}{2\epsilon_0} \hat{\mathbf{r}}$ ,  $\hat{\mathbf{r}}$  points perpendicularly to the plane


# A.10

## 7A


- (a) No
- (b)  $1/C_{\text{ser}} = 1/C_{\text{small}} + 1/C_{\text{large}} \approx 1/C_{\text{small}} \quad \therefore C_{\text{ser}} \approx C_{\text{small}}$
- (c) 2.556 pF
- (d) 10.89 pF

## 7B.1

(e)

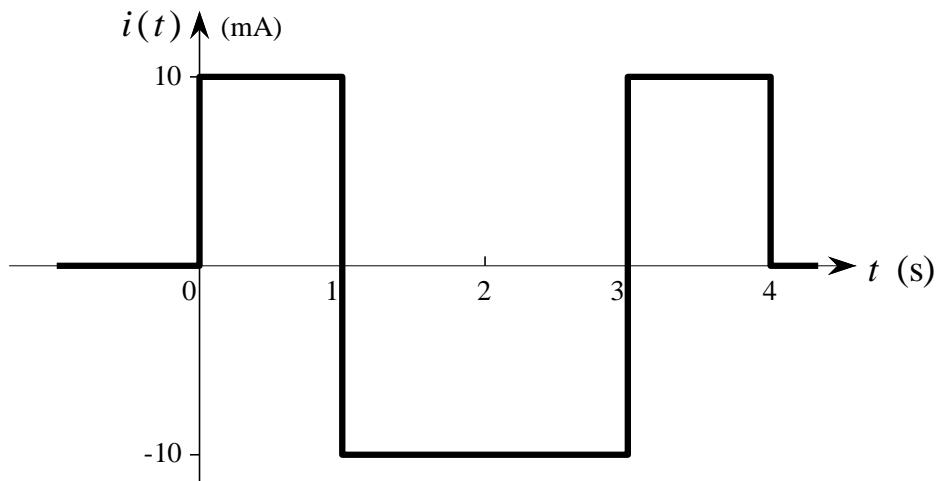

(f)

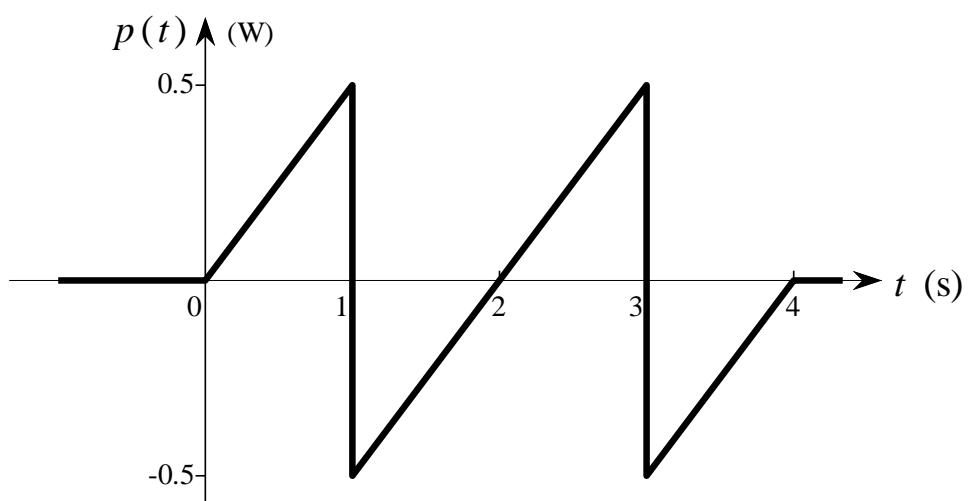

(g) 0.25 J

# A.12

## 8A

(a)  $L21 = 22 \mu\text{H}$


(b)  $T = 1 \mu\text{s}$

(c)  $I_p = 43.64 \text{ mA}$

(d)  $I_o = 21.82 \text{ mA}$

(e)  $20.95 \text{ mW}$

(f)

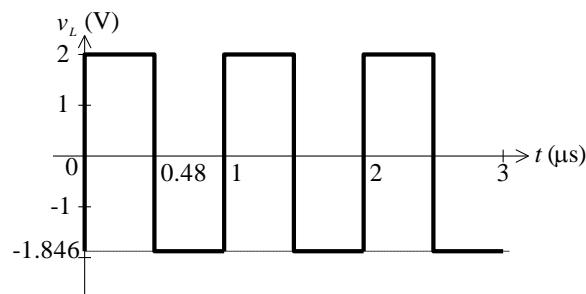

**8B.1**

- (a) 20.6 ms      (b) 177.7 ms

**8B.2**

- (a)  $60 \cos 10t$  V      (b)  $5 + 2 \sin 10t$  A

# A.14

## 9A

- (a) A = battery present, B = button working, C = energy harvester working  
G = green LED on, R = red LED on



(b)

A	B	C	G	R
0	0	0	0	0
0	0	1	0	1
0	1	0	0	0
0	1	1	0	1
1	0	0	0	1
1	0	1	1	1
1	1	0	1	0
1	1	1	1	0


(c)  $G = A\bar{B}C + AB\bar{C} + ABC$ ,  $R = \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C$

(d)  $G = A(B + C)$ ,  $R = A\bar{B} + \bar{A}C$

(e)

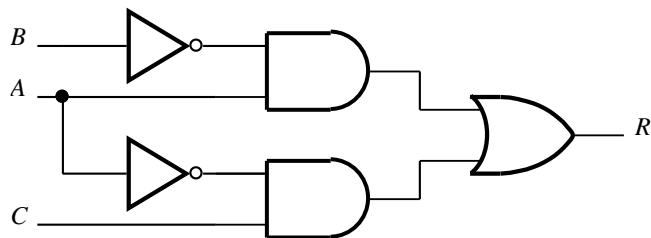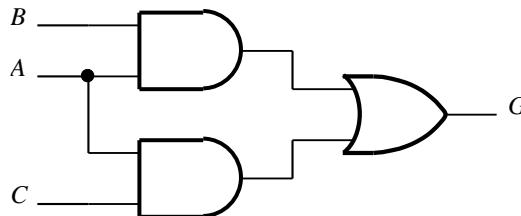

(f)

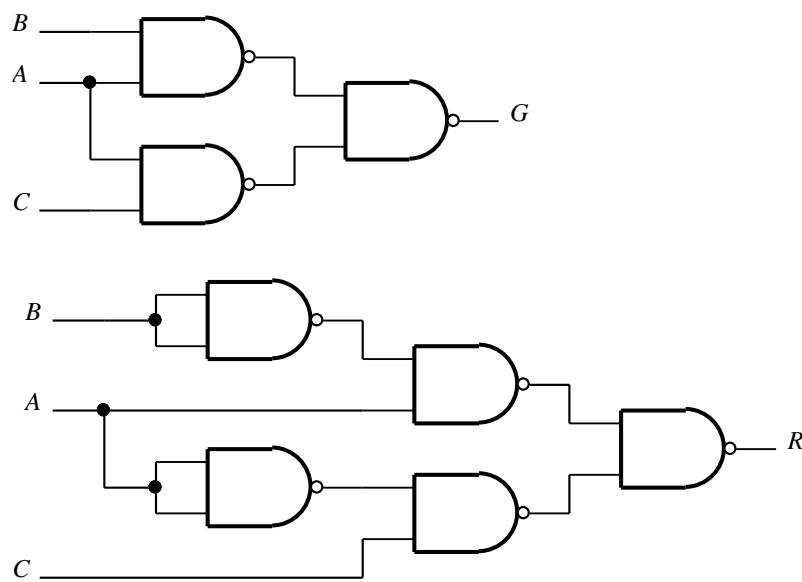


**9B.1**


$$L = (A + B)C$$

**9B.2**


(a)

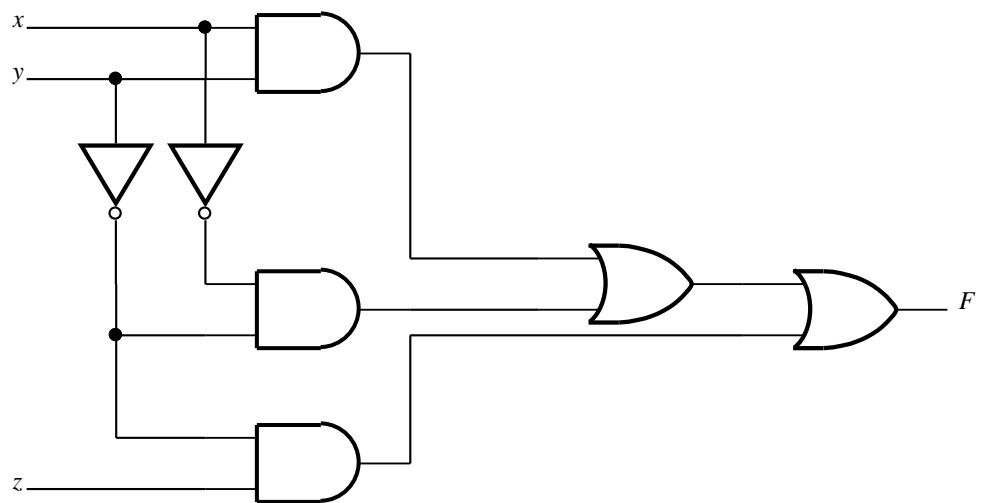


(b)

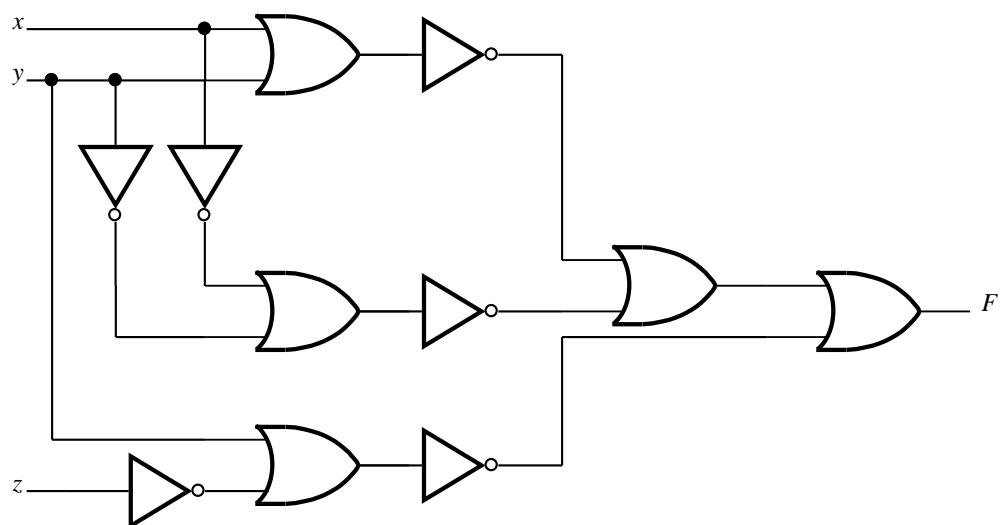

(c)

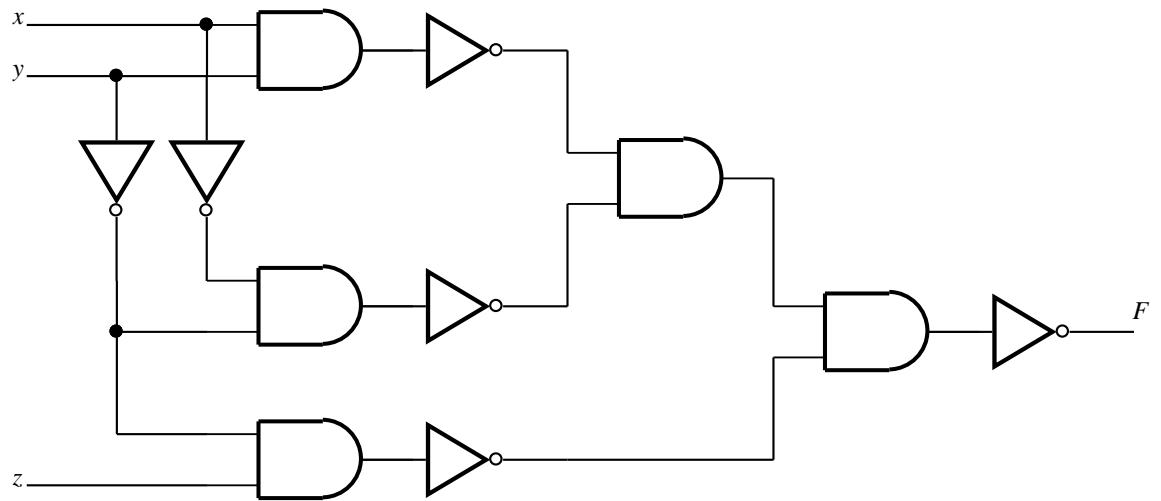


(d)

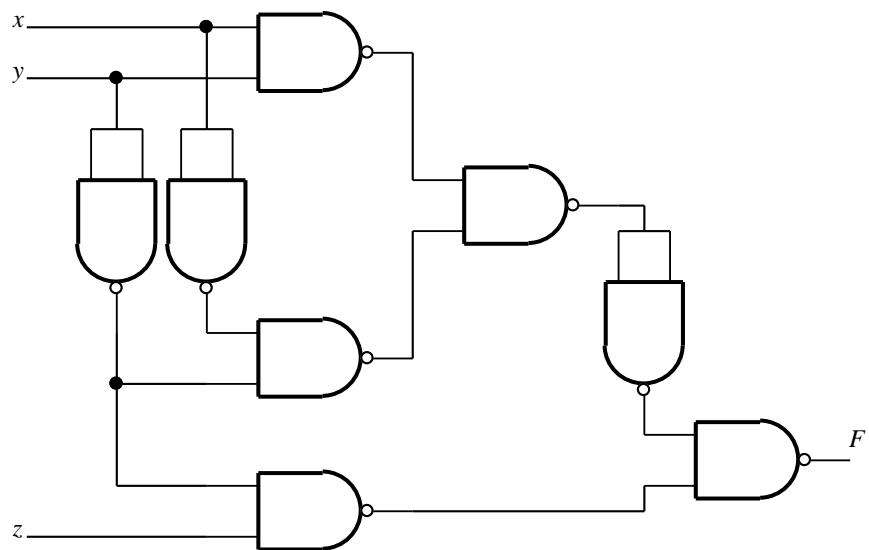

**10A**

(a)

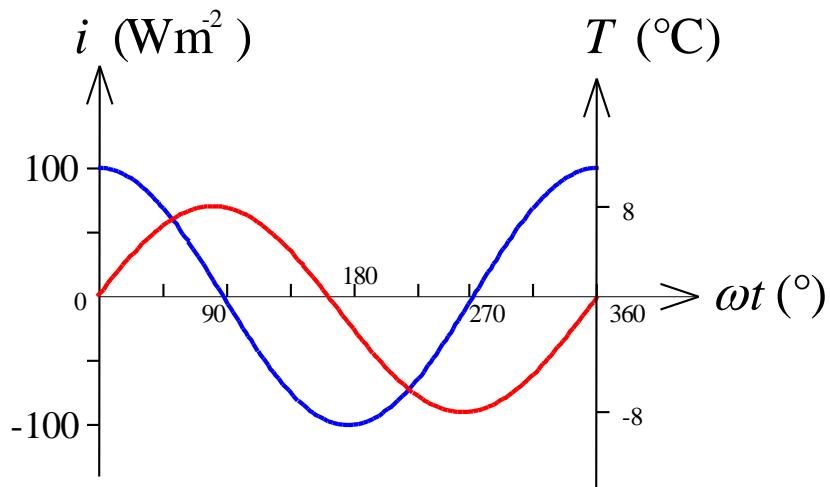

- (b)  $T = 52 \text{ weeks}$ ,  $\omega = \frac{2\pi}{52} \text{ rad/week}$ ,  $f = 31.80 \text{ nHz}$
- (c) Temperature deviation lags solar intensity deviation because its peak occurs later in time.
- (d)  $-90^\circ$
- (e)  $7.494 \text{ }^\circ\text{C}$
- (f)  $\mathbf{I} = 100 \angle 0^\circ$ ,  $\mathbf{T} = 80 \angle -90^\circ$

**10B.1**

- (a)  $i(t) = 5.51 \cos(314t - 33.8^\circ)$  A
- (b)  $i(5\text{m}) = 5.029 - 4.32 + 2.37 = 3.08$  A


**10B.2**

- (a)  $-1.5 \pm j1.323$ ,  $2\angle \pm 138.6^\circ$ ,  $2e^{\pm j138.6^\circ}$
- (b)  $4.088\angle 95.73^\circ$
- (c)  $3.768 - j10.53$
- (d)  $3.125\angle 85.65^\circ$
- (e)  $2.236\angle 63.43^\circ$ ,  $2.236\angle -116.6^\circ$
- (f)  $14.72\angle -50.93^\circ$

# A.20


## 11A

(a)

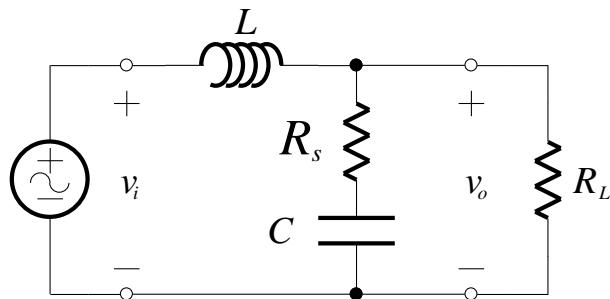

(b) 4 V

(c)

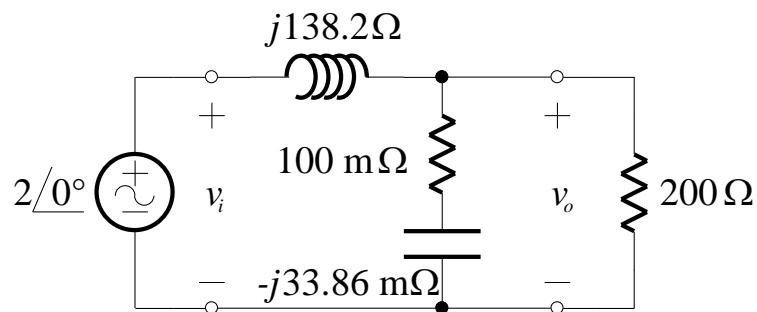

(d)  $7.662 \times 10^{-4}$

(e) -62.37 dB

**11B.1**

- (a)  $\mathbf{Z}_T = 3 - j4 = 5 \angle -53.13^\circ \Omega$
- (b)  $i(t) = 14.14 \cos(10^4 t - 36.87^\circ) \text{ A}$
- (c)  $v_R(t) = 42.42 \cos(10^4 t - 36.87^\circ) \text{ V}$   
 $v_L(t) = 84.84 \cos(10^4 t + 53.13^\circ) \text{ V}$   
 $v_C(t) = 141.4 \cos(10^4 t - 126.87^\circ) \text{ V}$
- (d)  $L = 0.8 \text{ mH}$
- (e) The impedance magnitude increases, consequently the peak value of current decreases. The phase angle changes to  $66.88^\circ$ , indicating that the current is *lagging* the voltage. The circuit has gone from being predominantly capacitive to predominantly inductive.

**11B.2**

- (a)  $395 \angle -1.5^\circ \text{ mA}$
- (b)  $0 \text{ V}$
- (c)  $90^\circ$
- (d)  $R = 12 \Omega$  in series with  $C = 50 \mu\text{F}$

**11B.3**

(a)

$$\begin{aligned}(5+j4)I_1 - (3+j4)I_2 &= 18\angle 80^\circ \\ -(3+j4)I_1 + (7+j)I_2 &= (4-j3)I_3 \\ I_3 &= -6\end{aligned}$$

(b)

$$\begin{aligned}(5+j4)I_1 - (3+j4)I_2 &= 18\angle 80^\circ \\ -(3+j4)I_1 + (7+j)I_2 &= -24 + j18\end{aligned}$$

(c)  $\mathbf{I}_1 = 4.194\angle 135.3^\circ \text{ A}, \mathbf{I}_2 = 6.669\angle 153.4^\circ \text{ A}$

(d)  $\mathbf{I}_A = 2.982\angle -0.6917^\circ \text{ A}$

(e)  $i_1(t) = 4.194\cos(314t + 135.3^\circ) \text{ A}, i_2(t) = 6.669\cos(314t + 153.4^\circ) \text{ A}$

(f)  $i_b(t) = 6.669 \cos(314t - 26.6^\circ) \text{ A}$